



# Relay Kickback Voltage Analysis

[www.electronicbeliever.com](http://www.electronicbeliever.com)

## Objective:


- ✓ To analyze kickback voltage on relay, derive working equations and perform simulation

## Topics:

- Model Circuit
- Analysis During ON Time
- Analysis During OFF Time
- Deriving the Maximum  $\Delta I$
- Deriving the  $\Delta t$
- Solving the Coil Voltage and VDS
- Simulations
- Reviewing What We Have Learned

## Relay Kickback Voltage Analysis


# Introduction

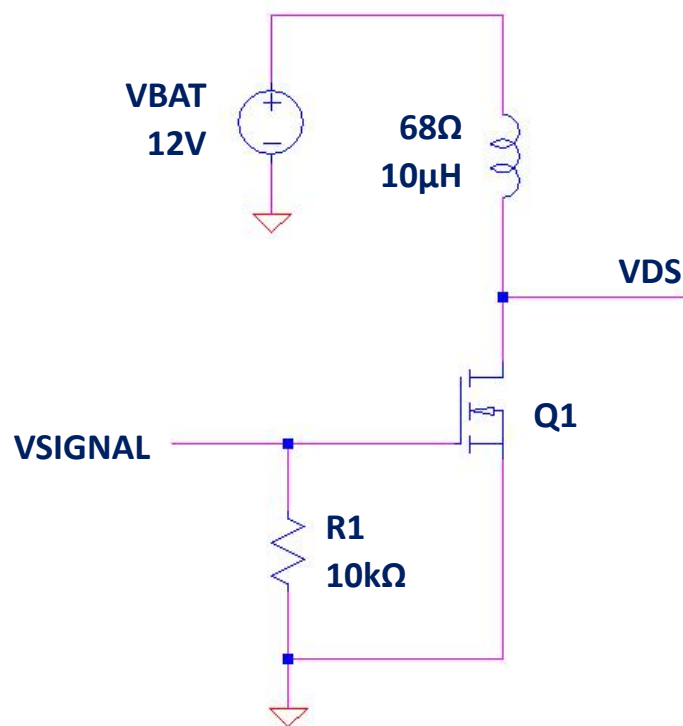

- ✓ Relays are commonly use to drive a high current load from a low voltage low current signal such as signals coming from MCU, DSC, DSP and other digital circuits
- ✓ Relay drivers are devices that drive the relay coil to change its contact state
- ✓ Relay driver is can be a MOSFET, BJT or opto-coupler

## Relay Kickback Voltage Analysis

# Model Circuit

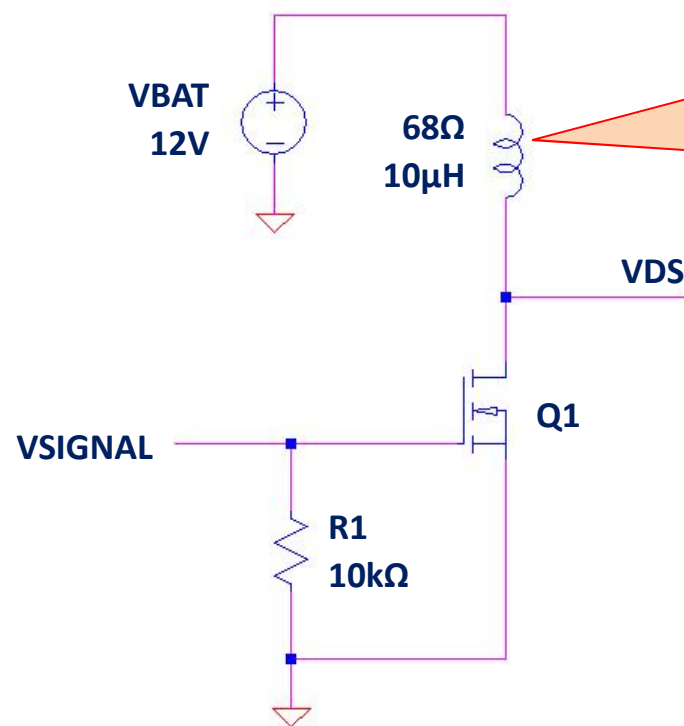


Relay coil with 68 ohm internal series resistance and 10uH inductance. The contact side is not anymore shown because it is not relevant in the analysis.

Drain-source voltage of the transistor Q1. The kickback voltage will be shown in this node.

When **VSIGNAL** is high, **Q1** will saturate and the **VDS** is ideally zero. Once **VSIGNAL** is turned low, **Q1** will turn off and this time the kickback voltage will occur.

## Relay Kickback Voltage Analysis

# Analysis During ON Time

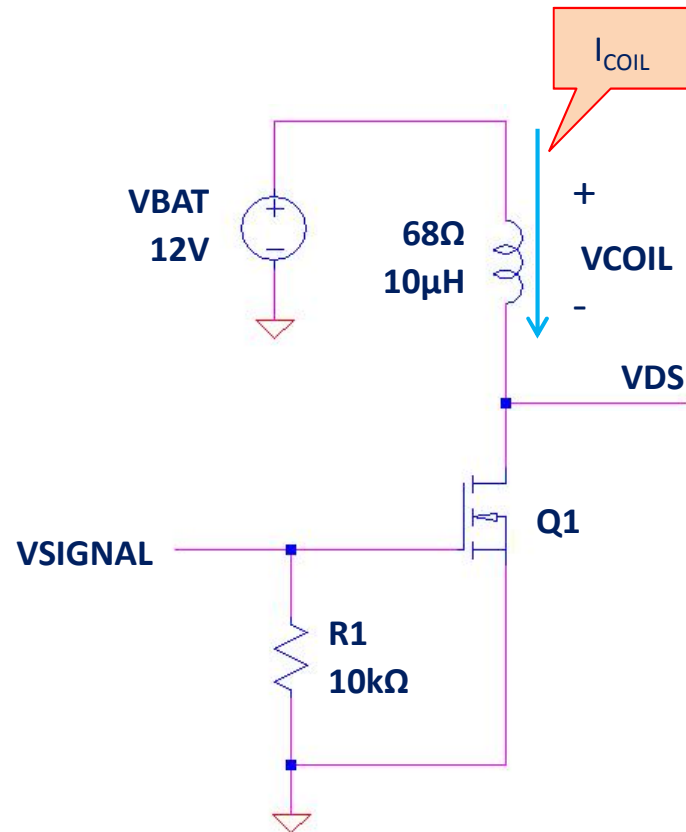

✓ When Q1 is ON, the current will flow from VBAT to the coil then to Q1 and return to the ground

✓ The current will flow as shown in the arrow direction

✓ During this time the upper side of the coil is positive while the lower side has negative sign

✓ During this time also, the VDS is approximately zero

$$VDS = VBAT - VCOIL$$


1

$$VDS = VQ1 \sim 0V$$

2

## Relay Kickback Voltage Analysis

# Analysis During OFF Time

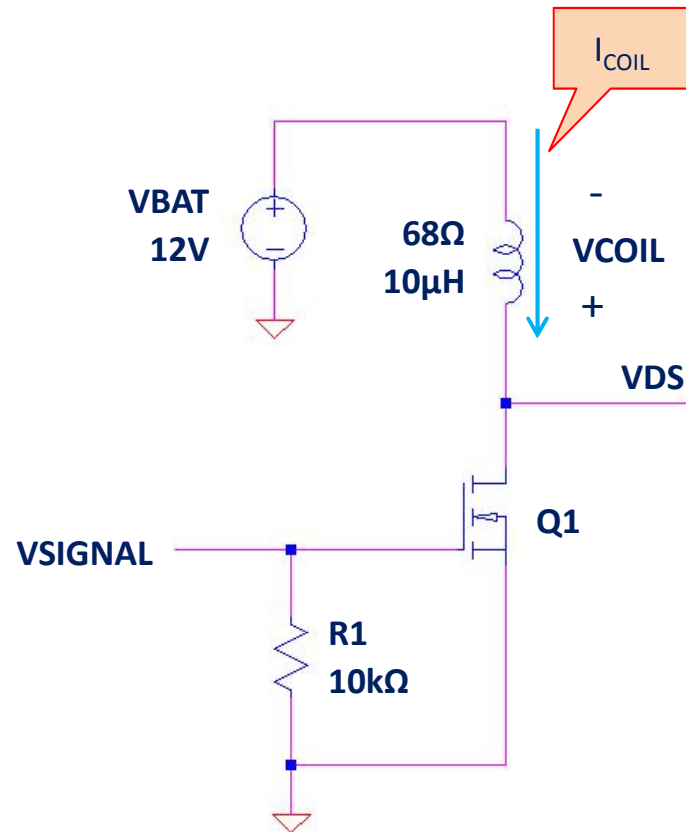

✓ When Q1 is OFF, there is a sudden change in the circuit current. However, the coil will not let it to happen immediately. It will maintain the current direction momentarily by reversing its polarity.

✓ During this time the upper side of the coil has negative sign while the lower side is positive


$$VBAT + V_{COIL} - V_{DS} = 0$$

$$V_{DS} = V_{BAT} + V_{COIL}$$

3

## Relay Kickback Voltage Analysis

# Analysis During OFF Time

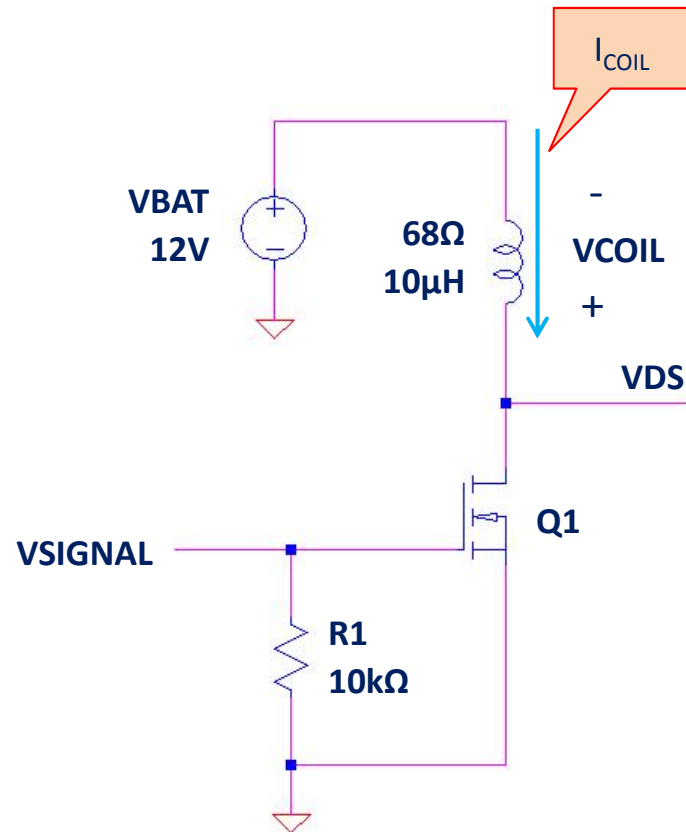

✓ From equation 3, the VDS which is the voltage seen by the MOSFET is the sum of VBAT and the coil voltage.

$$VDS = VBAT + VCOIL$$

3


Coil Voltage Equation

$$VCOIL = L \times \Delta i / \Delta t$$

4

## Relay Kickback Voltage Analysis

# Deriving the Maximum $\Delta i$

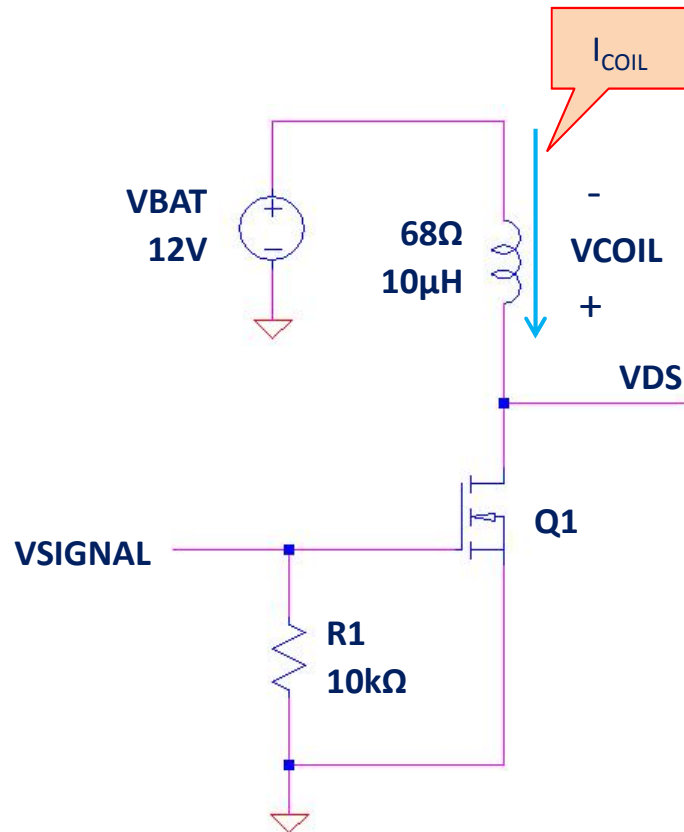

✓  $\Delta i$  is final current minus initial current. Final current would be zero and the initial current is the running current.

✓ Do not be confused if the  $\Delta i$  is negative. A negative sign just means that the inductor reverses its polarity


✓ The maximum value is can be  
(neglecting the drop of the  
I

$\Delta i$  is final cu $12V/68\Omega$ ) – 0A = 0.176 A  
urrent. Final



## Relay Kickback Voltage Analysis

## Deriving the $\Delta t$

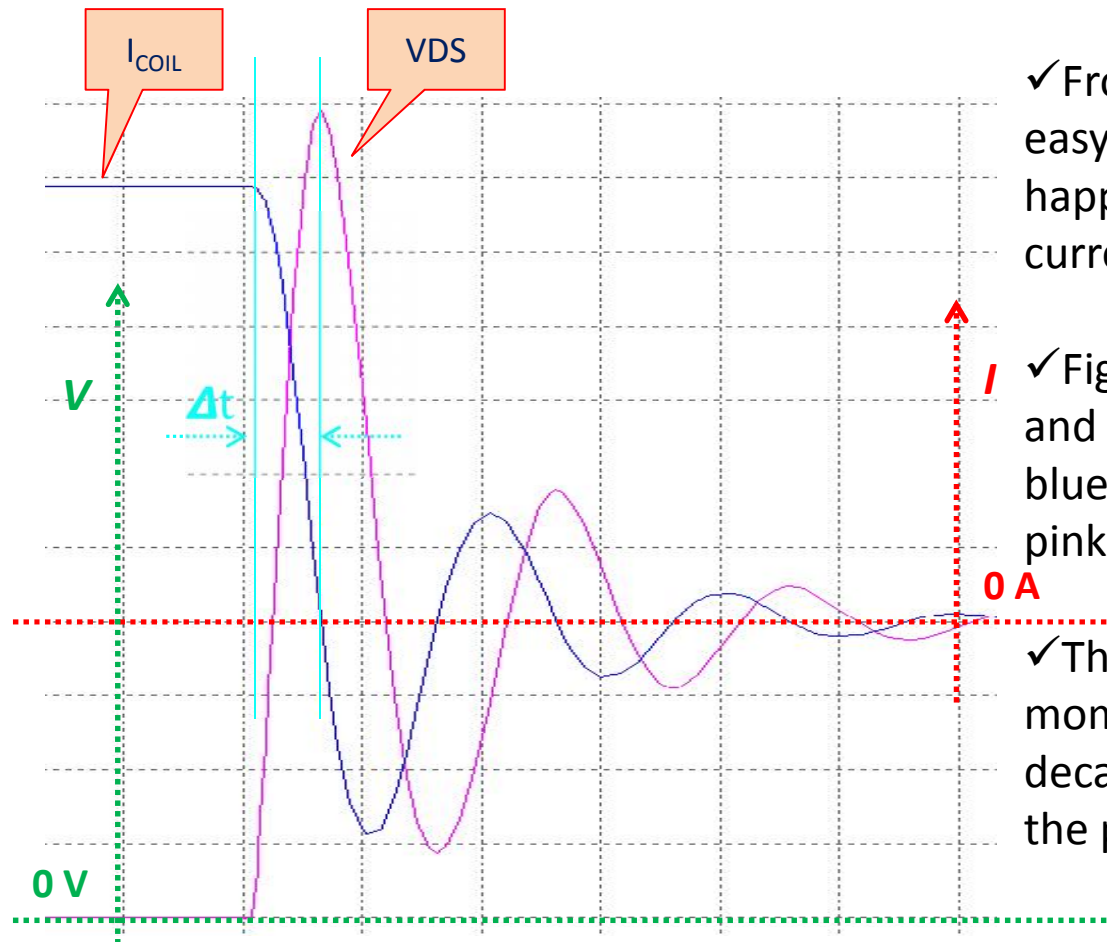


✓ From the coil voltage equation, it is easy to tell that the maximum level is happening at the maximum change in current

✓ Figure in the left is a simulated VDS and coil current. When the current (in blue) is at the zero level, the VDS (in pink) is at its peak level.

✓ The  $\Delta t$  is measured from the moment the coil current starts to decay until 0A wherein the VDS is at the peak level

## Relay Kickback Voltage Analysis

## Deriving the $\Delta t$

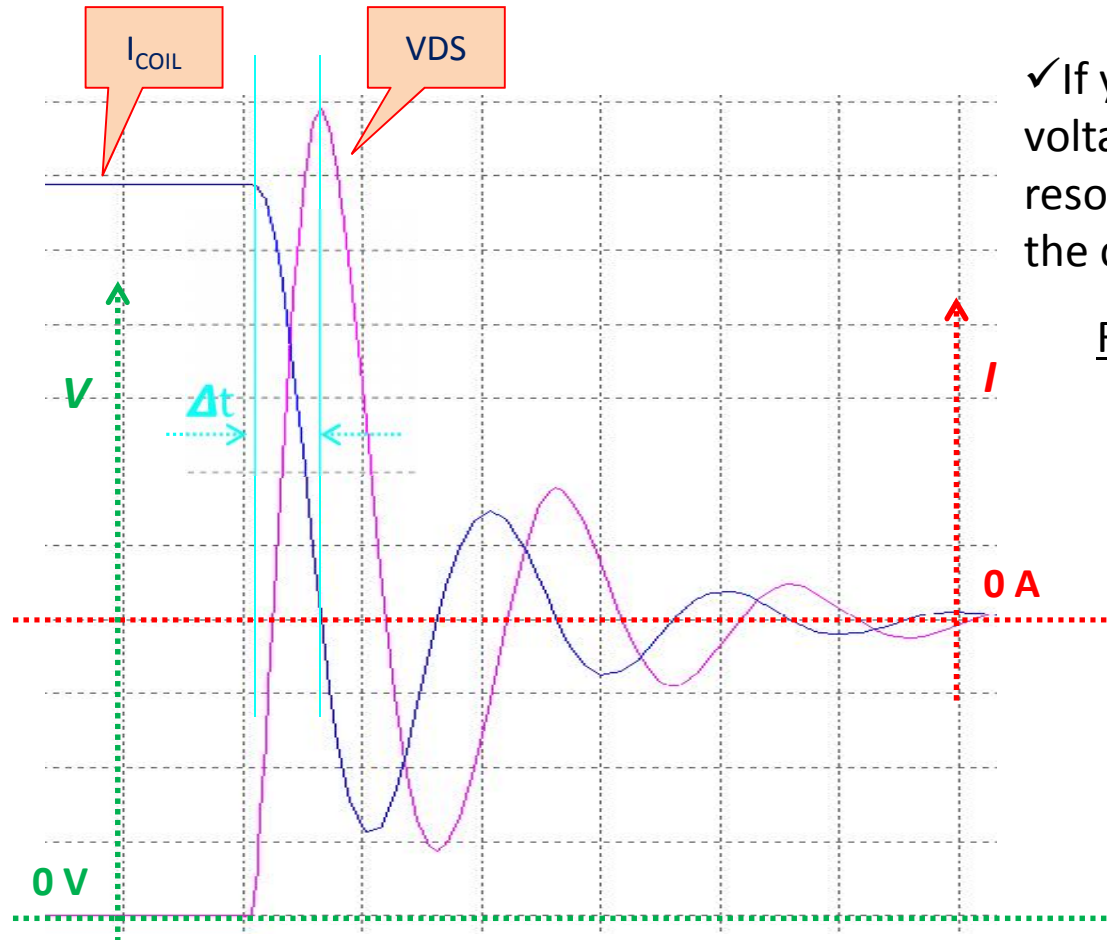

✓ If you wonder why the current and voltage oscillates; it's due to the resonance of the coil inductance and the capacitance of the MOSFET

### Resonance Frequency Equation

$$F_{\text{RESONANCE}} = \frac{1}{2\pi\sqrt{LC}}$$


5

#### Where

*L* is the coil inductance while *C* is the MOSFET output capacitance plus stray capacitances

## Relay Kickback Voltage Analysis

## Deriving the $\Delta t$

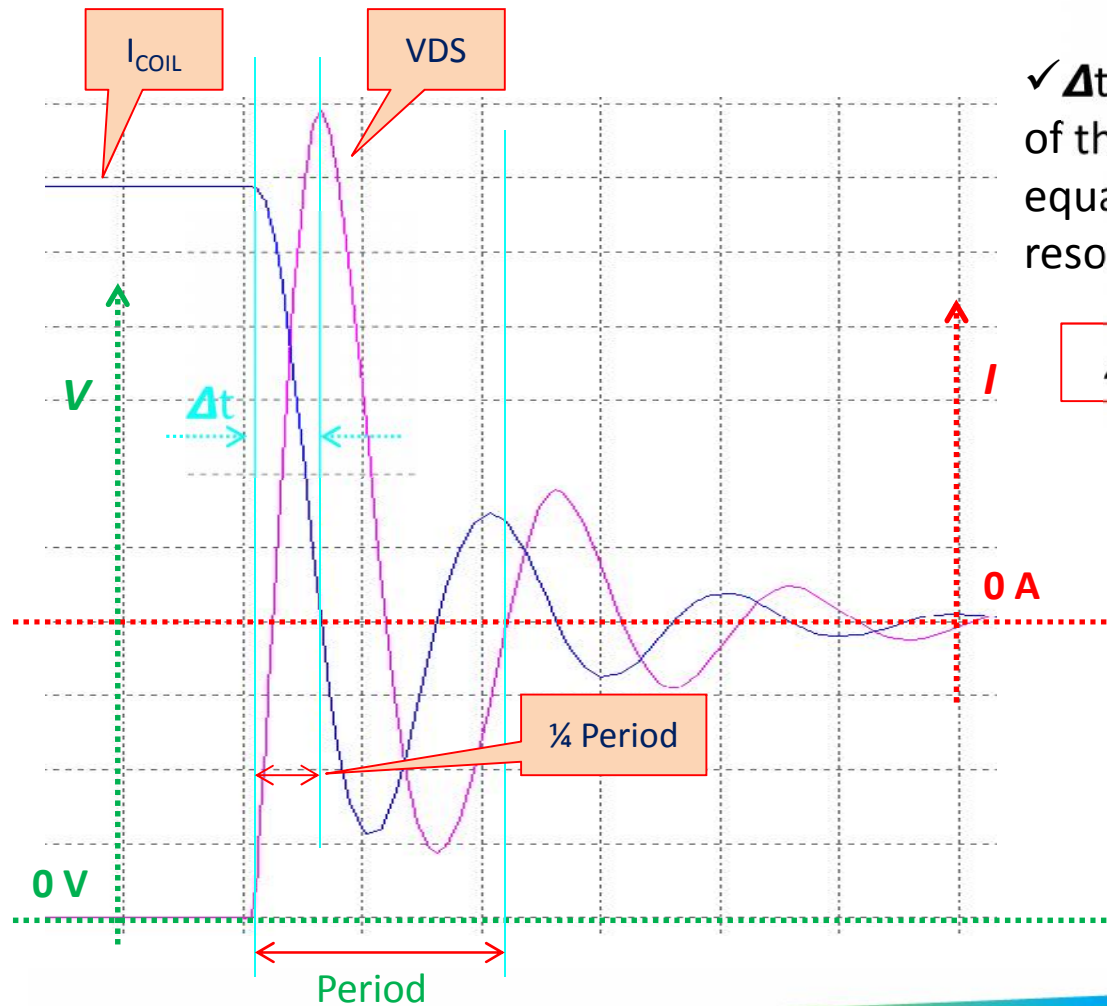


✓  $\Delta t$  is just  $\frac{1}{4}$  of the one cycle period of the oscillation. The period is just equal to the reciprocal of the resonance frequency.

$$\Delta t = \frac{1}{4} \times \left( \frac{1}{F_{\text{RESONANCE}}} \right)$$

6

## Relay Kickback Voltage Analysis

# Solving the Coil Voltage and VDS

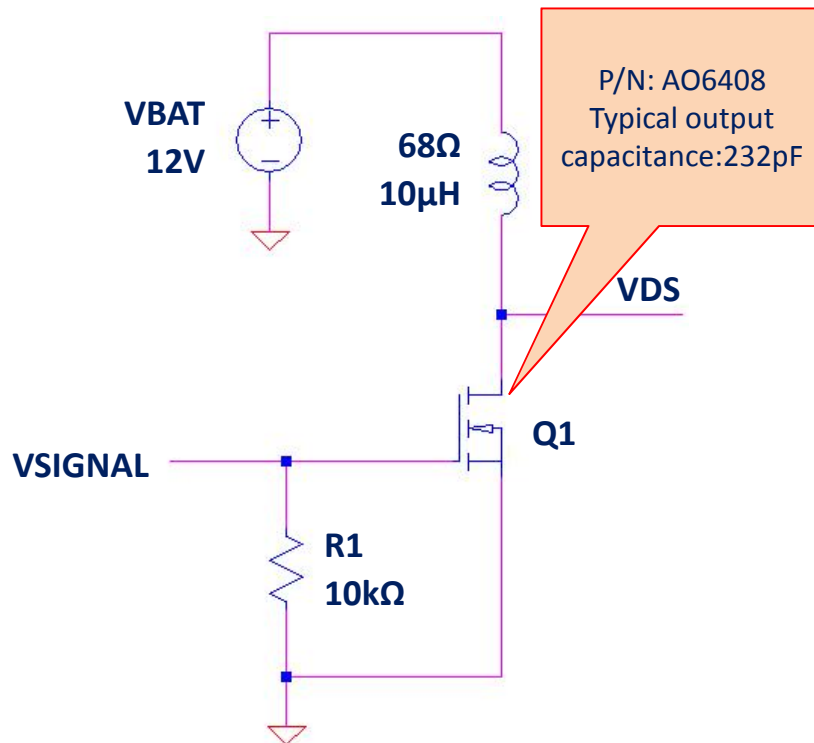

$$\Delta i_{\text{maximum}} = (12\text{V}/68\Omega) - 0\text{A} = \mathbf{0.176\text{ A}}$$

$$F_{\text{RESONANCE}} = \frac{1}{2\pi\sqrt{LC}}$$

$$F_{\text{RESONANCE}} = \mathbf{3.3043\text{ MHz}}$$

$$\text{Period} = 1/F_{\text{RESONANCE}} = \mathbf{302.64\text{ nsec}}$$



$$\Delta t = \frac{1}{4} \times \text{Period} = \mathbf{75.66\text{ nsec}}$$

$$V_{\text{COIL}} = L \times \Delta i / \Delta t = \mathbf{23.26\text{ V}}$$

$$V_{\text{DS}} = V_{\text{BAT}} + V_{\text{COIL}} = 12\text{V} + 23.26\text{ V} = \mathbf{35.26\text{V}}$$

# Relay Kickback Voltage Analysis

# Simulations

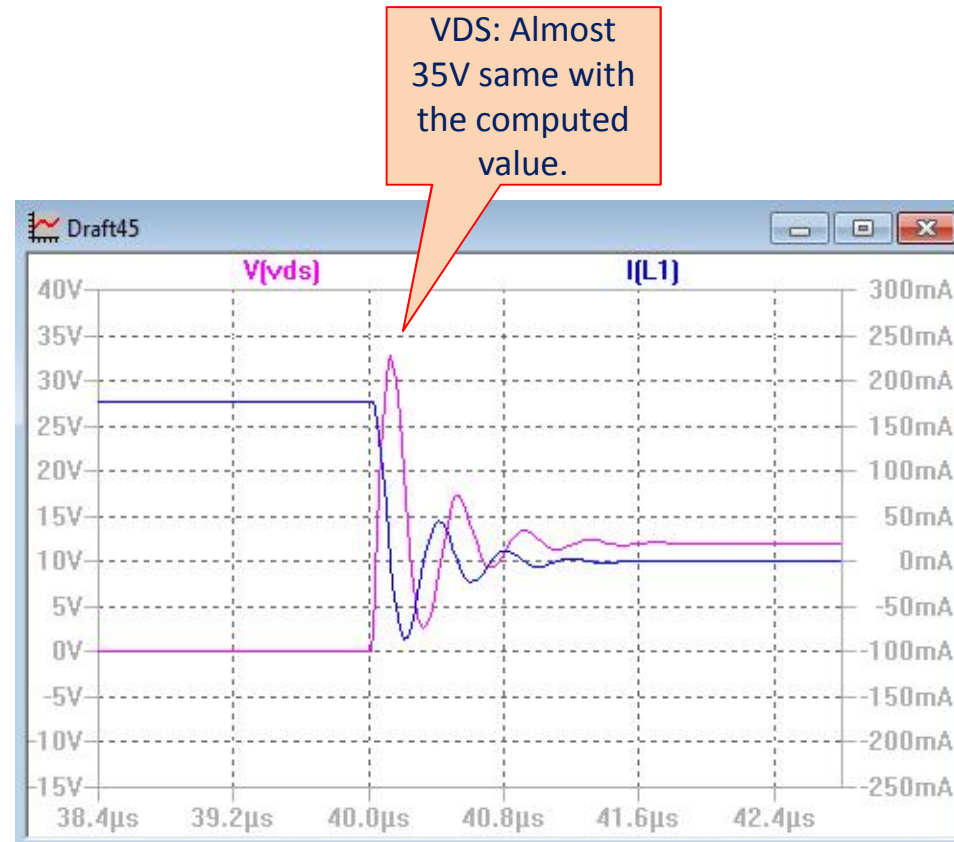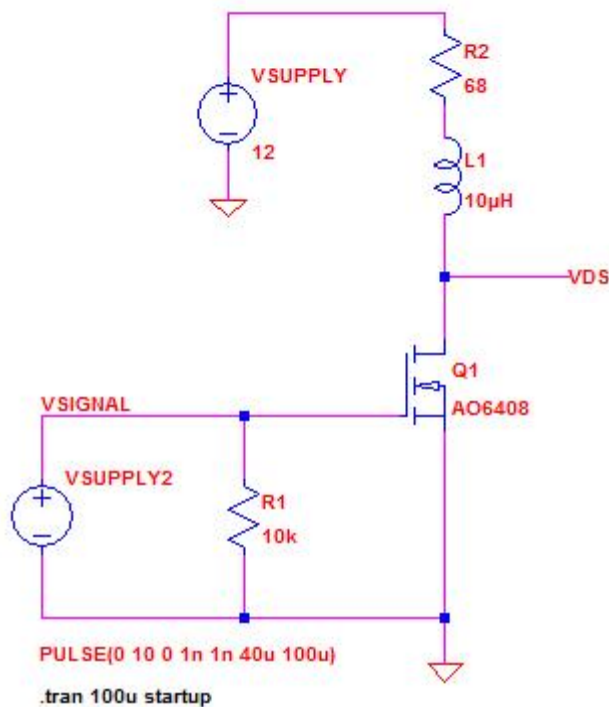

- ✓ Inductive kickback on relay is can be computed using simple circuit analysis
- ✓ The challenging part is how to get the change in time or  $\Delta t$
- ✓  $\Delta t$  is can be solved by studying the resonance of the coil inductance and the output capacitance of the MOSFET
- ✓ The change in time is measured from the moment the inductor current starts to decrease up to the time where the VDS is at its peak level
- ✓  $\Delta t$  is just  $\frac{1}{4}$  of the period of the oscillation of the coil inductance and the output capacitance

Reference:

<http://electronicsbeliever.com/?s=relay+kickback+voltage>

Visit [www.electronicbeliever.com](http://www.electronicbeliever.com) for more  
interesting topics