
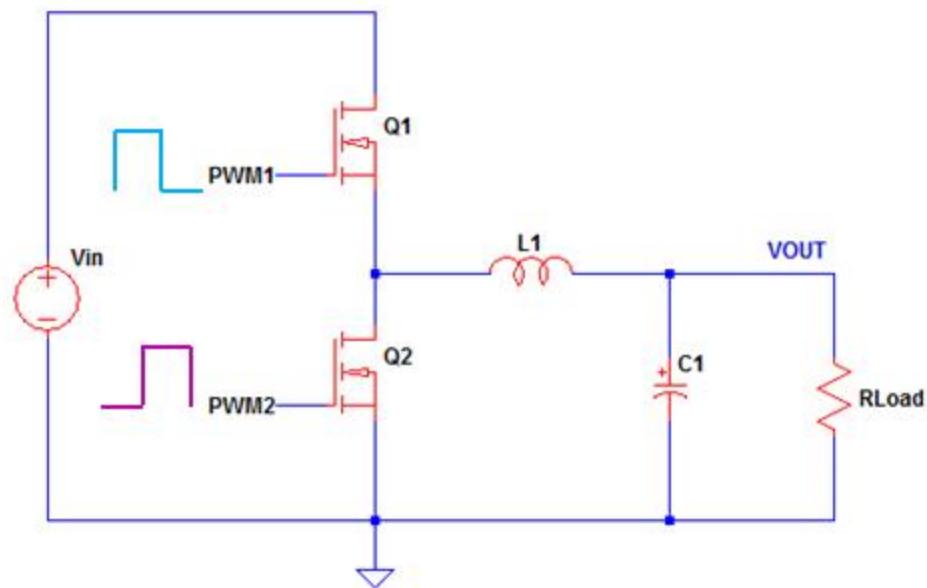


Synchronous Buck Converter Design

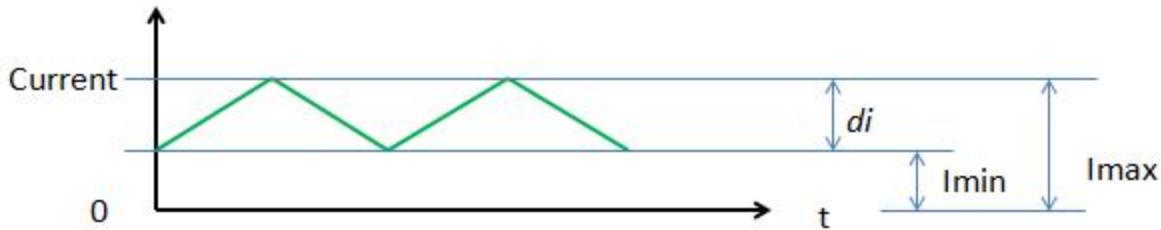

Derivations of Important Equations

Inductor Current Derivation



$$I_{DC_di} = \frac{di}{2}$$

$$I_{DC_total} = I_{min_DC} + I_{DC_di}$$

$$I_{min_DC} = \frac{1}{T_{sw}} \cdot \int_0^{T_{sw}} I_{min} dt \text{ simplify} \rightarrow I_{min_DC} = I_{min}$$

$$I_{min_DC} = I_{min}$$

$$di_{DC} = \frac{1}{T_{sw}} \cdot \int_0^{T_{sw}} \frac{t}{T_{sw}} \cdot di dt \text{ simplify} \rightarrow di_{DC} = \frac{di}{2}$$

$$di_{DC} = \frac{di}{2}$$

$$I_{DC_total} = I_{min} + \frac{di}{2}$$

$$I_{DC_total} = I_{max} - di + \frac{di}{2} \text{ solve, } I_{max} \rightarrow I_{DC_total} + \frac{di}{2}$$

$$I_{max} = I_{DC_total} + \frac{di}{2}$$

$$I_{max} = I_{load} + \frac{di}{2}$$

Note : The total DC current is equal to the DC of the load current

Inductor RMS Current

$$I_{RMS_inductor} = I_{RMS_di} + I_{min_RMS}$$

$$I_{RMS_di} = \sqrt{\frac{1}{T} \cdot \int_0^T \left(\frac{t}{T} \cdot di \right)^2 dt} \text{ simplify } \rightarrow I_{RMS_di} = \frac{\sqrt{3} \cdot \sqrt{di^2}}{3}$$

$$I_{RMS_di} = \frac{\sqrt{3} \cdot \sqrt{di^2}}{3}$$

$$I_{RMS_di} = \frac{di}{\sqrt{3}}$$

$$I_{min_RMS} = \sqrt{\frac{1}{T} \cdot \int_0^T I_{min}^2 dt} \text{ solve, } I_{min_RMS} \rightarrow \sqrt{I_{min}^2}$$

$$I_{min_RMS} = I_{min}$$

$$I_{RMS_inductor} = \frac{di}{\sqrt{3}} + I_{min}$$

$$I_{RMS_inductor} = \frac{di}{\sqrt{3}} + I_{max} - di$$

di Derivation (inductor ripple)

$$di = \int_{Ton}^T \frac{(V_{out} + V_D)}{L1} dt \text{ simplify } \rightarrow di = \frac{(T - Ton) \cdot (V_{out} + V_D)}{L1}$$

$$di = \frac{(T - Ton) \cdot (V_{out} + V_D)}{L1}$$

$$-(Ton - Tsw) \cdot (Vout + V_D) = -Ton \cdot (VQ1 - Vin + Vout) \text{ solve, } Vout \rightarrow \frac{V_D \cdot (Ton - Tsw) - Ton \cdot (VQ1 - Vin)}{Tsw}$$

$$Vout = \frac{V_D \cdot (Ton - Tsw) - Ton \cdot (VQ1 - Vin)}{Tsw}$$

$$Vout = \frac{V_D \cdot (Ton - Tsw) - Ton \cdot (VQ1 - Vin)}{Tsw} \text{ substitute, } Ton = D \cdot Tsw \rightarrow Vout = D \cdot Vin - D \cdot VQ1 - V_D + D \cdot V_D$$

$$Vout = D \cdot Vin - D \cdot VQ1 - V_D + D \cdot V_D$$

$$Vout = D \cdot Vin - D \cdot VQ1 - V_D + D \cdot V_D \text{ solve, } D \rightarrow \frac{Vout + V_D}{Vin - VQ1 + V_D}$$

$$D = \frac{Vout + V_D}{Vin - VQ1 + V_D} \text{ solve, } Vout \rightarrow D \cdot Vin - D \cdot VQ1 - V_D + D \cdot V_D$$

$$di = \int_0^{Ton} \frac{(Vin - VQ1 - Vout)}{L1} dt \text{ solve, } di \rightarrow -\frac{Ton \cdot (VQ1 - Vin + Vout)}{L1}$$

$$di = -\frac{Ton \cdot (VQ1 - Vin + Vout)}{L1} \text{ substitute, } Ton = D \cdot T \rightarrow di = -\frac{D \cdot T \cdot (VQ1 - Vin + Vout)}{L1}$$

$$di = -\frac{D \cdot T \cdot (VQ1 - Vin + Vout)}{L1}$$

$$Imin_RMS = \sqrt{\frac{1}{Tsw} \left(\int_0^{Ton} Imin^2 dt \right)} \text{ simplify} \rightarrow Imin_RMS = \sqrt{\frac{Imin^2 \cdot Ton}{Tsw}}$$

$$Imin_RMS = \sqrt{\frac{Imin^2 \cdot Ton}{Tsw}} \text{ substitute, } Ton = D \cdot Tsw \rightarrow Imin_RMS = \sqrt{D \cdot Imin^2}$$

$$\int_{T_{on}}^T \frac{(V_{out} + V_D)}{L_1} dt = \int_0^{T_{on}} \frac{(V_{in} - V_{Q1} - V_{out})}{L_1} dt$$

$$\frac{(T - T_{on}) \cdot (V_{out} + V_D)}{L_1} = -\frac{T_{on} \cdot (V_{Q1} - V_{in} + V_{out})}{L_1}$$


$$(T - T_{on}) \cdot (V_{out} + V_D) = -T_{on} \cdot (V_{Q1} - V_{in} + V_{out})$$

$$-T \cdot (D - 1) \cdot (V_{out} + V_D) = -D \cdot T \cdot (V_{Q1} - V_{in} + V_{out})$$

$$-T \cdot (D - 1) \cdot (V_{out} + V_D) = -D \cdot T \cdot (V_{Q1} - V_{in} + V_{out}) \text{ solve, } D \rightarrow \frac{V_{out} + V_D}{V_{in} - V_{Q1} + V_D}$$

$$D = \frac{V_{out} + V_D}{V_{in} - V_{Q1} + V_D} \quad D = \frac{V_{out}}{V_{in}}$$

Q1 Current Derivation

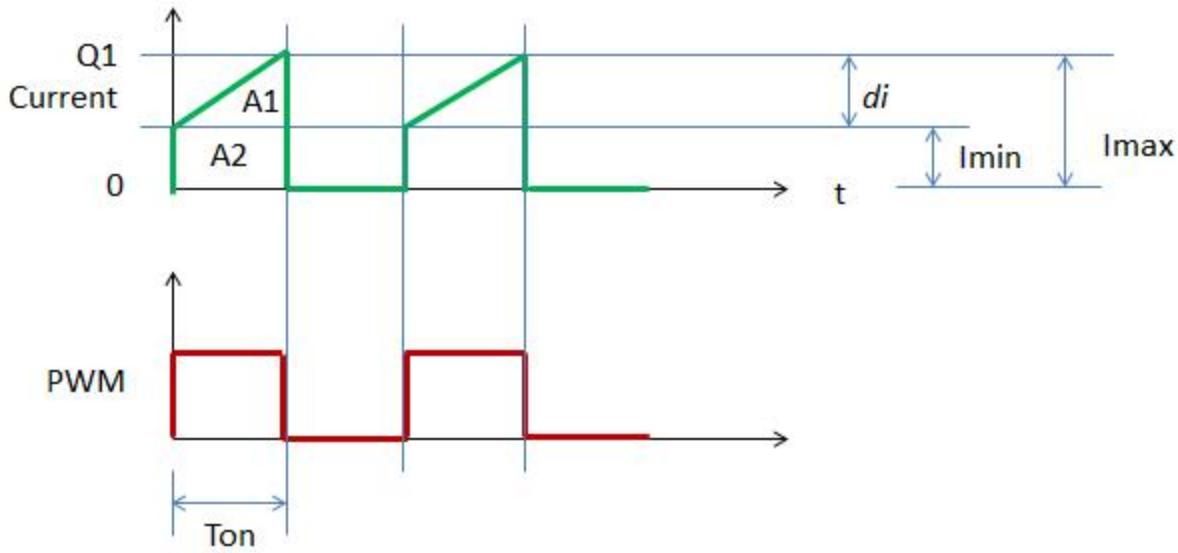

The RMS current of the switch is the sum of the RMS of the area \$A_1\$ and \$A_2\$. \$A_1\$ is a triangle while \$A_2\$ is rectangle.

RMS of Area A1

$$I_{RMS_A1} = \sqrt{\frac{1}{T} \int_0^{Ton} \left(\frac{di \cdot t}{Ton} \right)^2 dt} \text{ simplify } \rightarrow I_{RMS_A1} = \sqrt{\frac{3 \cdot Ton \cdot di^2}{3T}}$$

$$I_{RMS_A1} = \sqrt{\frac{3 \cdot Ton \cdot di^2}{3T}} \text{ substitute, } Ton = D \cdot T \rightarrow I_{RMS_A1} = \frac{\sqrt{3} \cdot \sqrt{D \cdot di^2}}{3}$$

$$I_{RMS_A1} = \frac{\sqrt{3} \cdot \sqrt{D \cdot di^2}}{3} \quad RMS \text{ of Area A2}$$

$$I_{RMS_A1} = di \cdot \sqrt{\frac{D}{3}}$$

$$I_{RMS_A2} = \sqrt{\frac{1}{T} \int_0^{Ton} Imin^2 dt} \text{ simplify } \rightarrow I_{RMS_A2} = \sqrt{\frac{Imin^2 \cdot Ton}{T}}$$

$$I_{RMS_A2} = \sqrt{\frac{Imin^2 \cdot Ton}{T}} \text{ substitute, } Ton = D \cdot T \rightarrow I_{RMS_A2} = \sqrt{D \cdot Imin^2}$$

$$I_{RMS_A2} = \sqrt{D \cdot Imin^2}$$

$$I_{RMS_A2} = Imin \cdot \sqrt{D}$$

RMS of the Switch Current

$$I_{RMS_Q1} = I_{RMS_A1} + I_{RMS_A2}$$

$$I_{RMS_Q1} = di \cdot \sqrt{\frac{D}{3}} + (Imax - di) \cdot \sqrt{D}$$

$$I_{RMS_Q1} = \sqrt{D} \cdot I_{max} - \sqrt{D} \cdot di + \frac{\sqrt{3} \cdot \sqrt{D} \cdot di}{3} \text{ solve, } I_{max} \rightarrow \frac{I_{RMS_Q1} + \sqrt{D} \cdot di - \frac{\sqrt{3} \cdot \sqrt{D} \cdot di}{3}}{\sqrt{D}}$$

$$I_{max} = \frac{I_{RMS_Q1} + \sqrt{D} \cdot di - \frac{\sqrt{3} \cdot \sqrt{D} \cdot di}{3}}{\sqrt{D}} \text{ simplify} \rightarrow I_{max} = di - \frac{\sqrt{3} \cdot di}{3} + \frac{I_{RMS_Q1}}{\sqrt{D}}$$

$$I_{max} = di - \frac{\sqrt{3} \cdot di}{3} + \frac{I_{RMS_Q1}}{\sqrt{D}}$$

$$I_{RMS_Q1} = di \cdot \sqrt{\frac{D}{3}} + (I_{max} - di) \cdot \sqrt{D} \text{ simplify} \rightarrow I_{RMS_Q1} = \sqrt{D} \cdot \left(I_{max} - di + \frac{\sqrt{3} \cdot di}{3} \right)$$

$$I_{RMS_Q1} = di \cdot \sqrt{\frac{D}{3}} + \left(I_{Load} + \frac{di}{2} - di \right) \cdot \sqrt{D} \text{ simplify} \rightarrow I_{RMS_Q1} = \sqrt{D} \cdot \left(I_{Load} - \frac{di}{2} + \frac{\sqrt{3} \cdot di}{3} \right)$$

Maximum Switch Current

$$I_{max} = di + I_{min}$$

Minimum Switch Current

$$I_{min} = I_{max} - di$$

Switch Average Current

$$I_{DC_A1} = \frac{1}{T_{sw}} \cdot \int_0^{T_{on}} \frac{di \cdot t}{T_{on}} dt \text{ simplify} \rightarrow I_{DC_A1} = \frac{T_{on} \cdot di}{2 \cdot T_{sw}}$$

$$I_{DC_A1} = \frac{T_{on} \cdot di}{2 \cdot T_{sw}} \text{ substitute, } T_{on} = D \cdot T_{sw} \rightarrow I_{DC_A1} = \frac{D \cdot di}{2}$$

$$I_{DC_A1} = \frac{D \cdot di}{2}$$

$$I_{DC_A2} = \frac{1}{T_{sw}} \int_0^{T_{on}} I_{min} dt \text{ simplify } \rightarrow I_{DC_A2} = \frac{I_{min} \cdot T_{on}}{T_{sw}}$$

$$I_{DC_A2} = \frac{I_{min} \cdot T_{on}}{T_{sw}} \text{ substitute, } T_{on} = D \cdot T_{sw} \rightarrow I_{DC_A2} = D \cdot I_{min}$$

$$I_{DC_A2} = D \cdot I_{min}$$

$$I_{DC_A2} = D \cdot (I_{max} - di)$$

$$I_{DC_total} = \frac{D \cdot di}{2} + D \cdot (I_{max} - di)$$

$$I_{DC_total} = I_{DC_A1} + I_{DC_A2}$$

$$I_{DC_total} = \frac{D \cdot di}{2} + D \cdot (I_{max} - di) \text{ simplify } \rightarrow I_{DC_total} = -\frac{D \cdot (di - 2 \cdot I_{max})}{2}$$

$$I_{DC_total} = -\frac{D \cdot (di - 2 \cdot I_{max})}{2}$$


$$I_{DC_total} = \frac{D \cdot (2 \cdot I_{max} - di)}{2}$$

$$I_{max} = I_{load} + di - \frac{D \cdot di}{2} \quad \text{from inductor current derivation}$$

$$I_{DC_total} = -\frac{D \left[di - 2 \cdot \left(I_{load} + di - \frac{D \cdot di}{2} \right) \right]}{2} \text{ simplify } \rightarrow I_{DC_total} = \frac{D \cdot (2 \cdot I_{load} + di - D \cdot di)}{2}$$

$$I_{DC_total} = \frac{D \cdot (2 \cdot I_{load} + di - D \cdot di)}{2}$$

Q2 Current Derivation

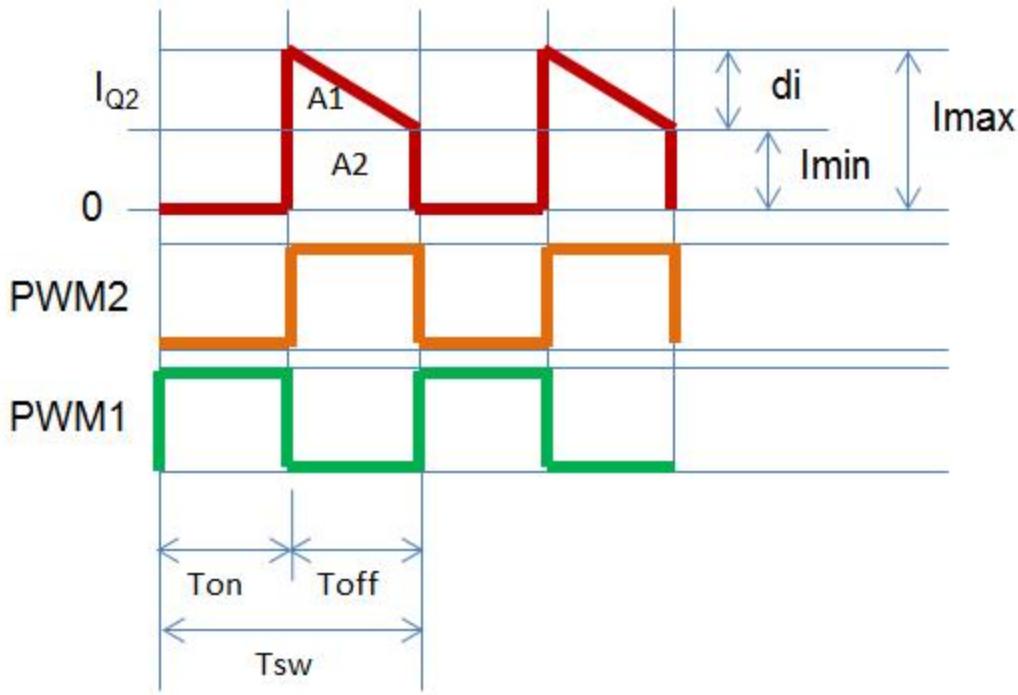

Q2 RMS Current

Q2 will conduct only at T_{off} .

$$I_{RMS_A1} = \sqrt{\frac{1}{T_{sw}} \cdot \int_{Ton}^{T_{sw}} \left(\frac{t - Ton}{T_{off}} \right)^2 \cdot di^2 dt} \text{ simplify } \rightarrow I_{RMS_A1} = \sqrt{\frac{3 \cdot di^2 \cdot (Ton - T_{sw})^3}{T_{sw} \cdot T_{off}^2}}$$

$$I_{RMS_A1} = \sqrt{\frac{3 \cdot di^2 \cdot (T_{sw} - Ton)^3}{T_{sw} \cdot T_{off}^2}} \text{ substitute, } T_{off} = T_{sw} - Ton \rightarrow I_{RMS_A1} = \sqrt{\frac{\sqrt{3} \cdot \sqrt{di^2 \cdot (Ton - T_{sw})}}{T_{sw}}}$$

$$I_{RMS_A1} = \sqrt{\frac{\sqrt{3} \cdot \sqrt{di^2 \cdot (T_{sw} - Ton)}}{T_{sw}}} \text{ substitute, } Ton = D \cdot T_{sw} \rightarrow I_{RMS_A1} = \sqrt{\frac{\sqrt{3} \cdot \sqrt{-di^2 \cdot (D - 1)}}{3}}$$

400W Synchronous Buck

$$I_{RMS_A1} = \frac{\sqrt{3} \cdot \sqrt{-di^2 \cdot (D - 1)}}{3}$$

$$I_{RMS_A1} = di \cdot \sqrt{\frac{1 - D}{3}}$$

$$I_{RMS_A2} = \sqrt{\frac{1}{T_{sw}} \cdot \int_{T_{on}}^{T_{sw}} I_{min}^2 dt} \text{ simplify } \rightarrow I_{RMS_A2} = \sqrt{-\frac{I_{min}^2 \cdot (T_{on} - T_{sw})}{T_{sw}}}$$

$$I_{RMS_A2} = \sqrt{-\frac{I_{min}^2 \cdot (T_{on} - T_{sw})}{T_{sw}}} \text{ substitute, } T_{on} = D \cdot T_{sw} \rightarrow I_{RMS_A2} = \sqrt{-I_{min}^2 \cdot (D - 1)}$$

$$I_{RMS_A2} = I_{min} \cdot \sqrt{(1 - D)}$$

$$I_{RMS_Q2} = I_{RMS_A1} + I_{RMS_A2}$$

$$I_{RMS_Q2} = di \cdot \sqrt{\frac{1 - D}{3}} + (I_{max} - di) \cdot \sqrt{1 - D}$$

$$I_{max_Q2} = I_{RMS_Q2} + di \cdot \left(1 - \sqrt{\frac{1 - D}{3}} \right)$$

$$I_{RMS_Q2} = \sqrt{1 - D} \cdot \left(I_{max} - di + \frac{\sqrt{3} \cdot di}{3} \right)$$

Q2 DC Current

$$I_{DC_A1} = \frac{1}{T_{sw}} \cdot \int_{T_{on}}^{T_{sw}} \left(\frac{t - T_{on}}{T_{off}} \right) \cdot di dt \text{ simplify } \rightarrow I_{DC_A1} = \frac{di \cdot (T_{on} - T_{sw})^2}{2 \cdot T_{sw} \cdot T_{off}}$$

$$I_{DC_A1} = \frac{di \cdot (T_{sw} - T_{on})^2}{2 \cdot T_{sw} \cdot T_{off}} \text{ substitute, } T_{off} = T_{sw} - T_{on} \rightarrow I_{DC_A1} = -\frac{T_{on} \cdot di - T_{sw} \cdot di}{2 \cdot T_{sw}}$$

$$I_{DC_A1} = \frac{T_{sw} \cdot di - T_{on} \cdot di}{2 \cdot T_{sw}} \text{ substitute, } T_{on} = D \cdot T_{sw} \rightarrow I_{DC_A1} = -\frac{di \cdot (D - 1)}{2}$$

$$I_{DC_A1} = -\frac{di \cdot (D - 1)}{2}$$

$$I_{DC_A1} = \frac{di \cdot (1 - D)}{2}$$

$$I_{DC_A2} = \frac{1}{T_{sw}} \cdot \int_{T_{on}}^{T_{sw}} I_{min} dt \text{ simplify} \rightarrow I_{DC_A2} = -\frac{I_{min} \cdot (T_{on} - T_{sw})}{T_{sw}}$$

$$I_{DC_A2} = -\frac{I_{min} \cdot (T_{on} - T_{sw})}{T_{sw}} \text{ substitute, } T_{on} = D \cdot T_{sw} \rightarrow I_{DC_A2} = -I_{min} \cdot (D - 1)$$

$$I_{DC_A2} = I_{min} \cdot (1 - D)$$

$$I_{DC_A2} = (I_{max} - di) \cdot (1 - D)$$

$$I_{DC_Q2} = \frac{di \cdot (1 - D)}{2} + (I_{max} - di) \cdot (1 - D)$$

MOSFETs Drain-Source Voltage

$$V_{Q1_Vinmax} = V_{in_max}$$

$$V_{Q1_Vinmin} = V_{in_min}$$

$$V_{Q2_Vinmax} = V_{in_max}$$

$$V_{Q2_Vinmin} = V_{in_min}$$

Calculations with Values

This section computes the currents of Q1, Q2 and L1. The resulting currents are total currents on the individual location. For instance, there are more than one MOSFETs used the Q1 slot, the current will be divided to how many MOSFETs on this slot.

Given Values

The maximum input power is 400W. The target efficiency is 95%. So, the output power will be

$$Pin := 400W$$

$$Eff := 95\%$$

$$Pout := Pin \cdot Eff$$

$$Pout = 380 W$$

With a 1 ohm resistor, the equivalent load current and voltage will be

$$RLoad := 1\Omega$$

Given load resistance used in the evaluation

$$I_Load := \sqrt{\frac{Pout}{RLoad}}$$

$$I_Load = 19.494 A$$

This is the computed load current

The output voltage is therefore

$$Vout := I_Load \cdot RLoad$$

$$Vout = 19.494 V$$

This is the computed output voltage of the converter

$$Vin_{max} := 100V$$

This is the maximum input voltage

$$Vin_{min} := 60V$$

Minimum input voltage

$$Fsw := 140kHz$$

Switching frequency of operation

$$L1 := 10\mu H$$

Selected inductance value

$$Cout := 880\mu F$$

Minimum output capacitance used

$$VQ1 := 0.2V$$

VQ1 and VQ2, approximated individual voltage drop of MOSFET in Q1 and Q2 slots

$$VQ2 := 0.2V$$

Equations Used

Maximum Input Voltage

$$T_{sw} := \frac{1}{F_{sw}}$$

$$D_{Vinmax} := \frac{V_{out} + V_{Q2}}{V_{in_max} - V_{Q1} + V_{Q2}}$$

$$di_{Vinmax} := -\frac{D_{Vinmax} \cdot T_{sw} \cdot (V_{Q1} - V_{in_max} + V_{out})}{L_1} \quad I_{max_Vinmax} := I_{Load} + \frac{di_{Vinmax}}{2}$$

$$I_{min_Vinmax} := I_{max_Vinmax} - di_{Vinmax}$$

$$I_{DC_Q2_Vinmax} := \frac{di_{Vinmax} \cdot (1 - D_{Vinmax})}{2} + (I_{max_Vinmax} - di_{Vinmax}) \cdot (1 - D_{Vinmax})$$

$$I_{RMS_Q2_Vinmax} := \sqrt{1 - D_{Vinmax}} \cdot \left(I_{max_Vinmax} - di_{Vinmax} + \frac{\sqrt{3} \cdot di_{Vinmax}}{3} \right)$$

$$I_{DC_Q1_Vinmax} := \frac{D_{Vinmax} \cdot di_{Vinmax}}{2} + D_{Vinmax} \cdot (I_{max_Vinmax} - di_{Vinmax})$$

$$I_{RMS_Q1_Vinmax} := di_{Vinmax} \cdot \sqrt{\frac{D_{Vinmax}}{3}} + (I_{max_Vinmax} - di_{Vinmax}) \cdot \sqrt{D_{Vinmax}}$$

$$I_{RMS_L1_Vinmax} := \frac{di_{Vinmax}}{\sqrt{3}} + I_{max_Vinmax} - di_{Vinmax} \quad V_{ripple_Vinmax} := di_{Vinmax} \cdot \frac{\frac{1}{F_{sw}}}{C_{out}}$$

$$\text{OperationMode_Vinmax} := \begin{cases} "CCM" & \text{if } I_{min_Vinmax} > 0 \\ "Boundary" & \text{if } I_{min_Vinmax} = 0 \\ ""DCM"" & \text{otherwise} \end{cases}$$

$$I_{rip_outcap_Vinmax} := \sqrt{I_{RMS_L1_Vinmax}^2 - I_{Load}^2}$$

Minimum Input Voltage

$$D_{Vinmin} := \frac{Vout + VQ2}{Vin_{min} - VQ1 + VQ2}$$

$$di_{Vinmin} := -\frac{D_{Vinmin} \cdot Tsw \cdot (VQ1 - Vin_{min} + Vout)}{L1} \quad Imax_{Vinmin} := I_{Load} + \frac{di_{Vinmin}}{2}$$

$$Imin_{Vinmin} := Imax_{Vinmin} - di_{Vinmin}$$

$$I_{DC_Q2_Vinmin} := \frac{di_{Vinmin} \cdot (1 - D_{Vinmin})}{2} + (Imax_{Vinmin} - di_{Vinmin}) \cdot (1 - D_{Vinmin})$$

$$I_{RMS_Q2_Vinmin} := \sqrt{1 - D_{Vinmin}} \left(Imax_{Vinmin} - di_{Vinmin} + \frac{\sqrt{3} \cdot di_{Vinmin}}{3} \right)$$

$$I_{DC_Q1_Vinmin} := \frac{D_{Vinmin} \cdot di_{Vinmin}}{2} + D_{Vinmin} \cdot (Imax_{Vinmin} - di_{Vinmin})$$

$$I_{RMS_Q1_Vinmin} := di_{Vinmin} \cdot \sqrt{\frac{D_{Vinmin}}{3}} + (Imax_{Vinmin} - di_{Vinmin}) \cdot \sqrt{D_{Vinmin}}$$

$$I_{RMS_L1_Vinmin} := \frac{di_{Vinmin}}{\sqrt{3}} + Imax_{Vinmin} - di_{Vinmin} \quad Vripple_{Vinmin} := di_{Vinmin} \cdot \frac{1}{Fsw \cdot Cout}$$

$$\text{OperationMode}_{Vinmin} := \begin{cases} "CCM" & \text{if } Imin_{Vinmin} > 0 \\ "Boundary" & \text{if } Imin_{Vinmin} = 0 \\ ""DCM"" & \text{otherwise} \end{cases}$$

$$VQ1_{Vinmax} := Vin_{max}$$

$$VQ1_{Vinmin} := Vin_{min}$$

$$VQ2_{Vinmax} := Vin_{max}$$

$$VQ2_{Vinmin} := Vin_{min}$$

$$I_{rip_outcap_Vinmin} := \sqrt{{I_{RMS_L1_Vinmin}}^2 - {I_{Load}}^2}$$

Computed Results

Maximum Input Voltage

OperationMode_Vinmax = "CCM"

$T_{sw} = 7.143 \cdot \mu s$

$D_{Vinmax} = 19.694 \cdot \%$

Duty cycle

$i_{di_Vinmax} = 11.297 \cdot A$

Inductor ripple current

$I_{min_Vinmax} = 13.845 \cdot A$

Minimum inductor current

$I_{max_Vinmax} = 25.142 A$

Repetitive peak current of inductor, diode and switch/controller

$I_{DC_Q2_Vinmax} = 15.655 A$

diode DC current

$I_{RMS_Q2_Vinmax} = 18.252 A$

RMS current of the diode

$I_{DC_Q1_Vinmax} = 3.839 A$

Switch DC current

$I_{RMS_Q1_Vinmax} = 9.039 A$

RMS current of the switch/controller

$I_{RMS_L1_Vinmax} = 20.367 A$

Inductor RMS current

$V_{ripple_Vinmax} = 91.693 \cdot mV$

Output ripple voltage

$I_{rip_outcap_Vinmax} = 5.902 A$

This is the total ripple current on the output capacitors. This will be divided by the number of output capacitor used.

Minimum Input Voltage

 $\text{OperationMode_Vinmin} = \text{"CCM"}$ $T_{sw} = 7.143 \cdot \mu\text{s}$ $D_{Vinmin} = 32.823\%$

Duty cycle

 $i_{di_Vinmin} = 9.45 \cdot A$

Inductor ripple current

 $I_{min_Vinmin} = 14.769 \cdot A$

Minimum inductor current

 $I_{max_Vinmin} = 24.218 A$

Repetitive peak current of inductor, diode and switch/controller

 $I_{DC_Q2_Vinmin} = 13.095 A$

diode DC current

 $I_{RMS_Q2_Vinmin} = 16.576 A$

RMS current of the diode

 $I_{DC_Q1_Vinmin} = 6.398 A$

Switch DC current

 $I_{RMS_Q1_Vinmin} = 11.587 A$

RMS current of the switch/controller

 $I_{RMS_L1_Vinmin} = 20.225 A$

Inductor RMS current

 $V_{ripple_Vinmin} = 0.077 \cdot V$

Output ripple voltage

 $I_{rip_outcap_Vinmin} = 5.388 A$

This is the total ripple current on the output capacitors. This will be divided by the number of output capacitor used.

Component Selection

For better matching, the upper and lower MOSFET must be of the same type. Below computations are individual losses in each MOSFET used in the Q1 and Q2 slots.

Q1 and Q2 Slot

1. The maximum voltage at least typical without considering the ringing for Q1 and Q2 slots is 100V which is the maximum input voltage. Based on experienced, ringing is can be as high as 70%, so a 200V MOSFET is a good choice.
2. The MOSFET RD_{Son} should be minimum so that the efficiency target of 95% is attainable
3. The dynamic paramters are must be small as well for efficiency reason


MOSFET Parameters (From the Datasheet)

$\text{RD}_{\text{Son}} := 0.034\Omega$

This is the drain to source on state resistance of the MOSFET. Multiplied this with the normalized value if only typical is provided.

$\text{RD}_{\text{Son_norm}} := 1.6$

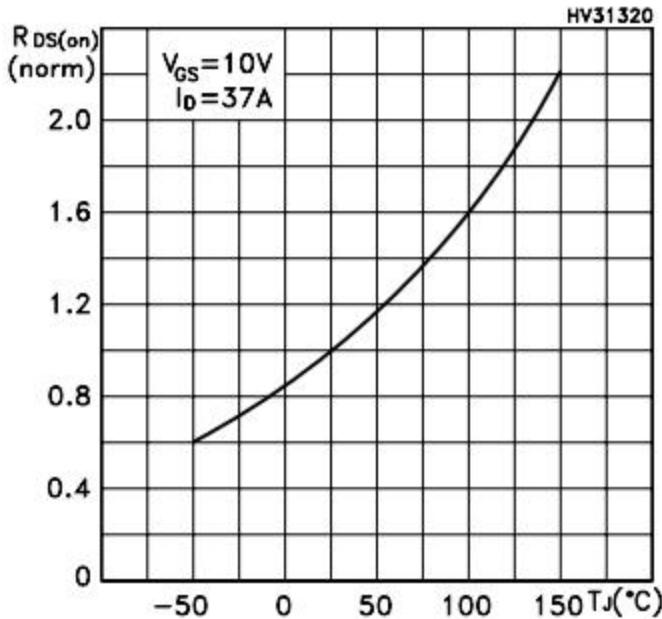This is the normalized RD_{Son} of the MOSFET. Use the value at 100°C.



$Q_{\text{gtotal}} := 84\text{nC}$

Maximum total gate charge of the MOSFET

Table 5. Dynamic

Symbol	Parameter	Test conditions	Min.	Typ.	Max.	Unit
$g_{fs}^{(1)}$	Forward transconductance	$V_{DS} = 15V, I_D = 37A$		40		S
C_{iss}	Input capacitance	$V_{DS} = 25V, f = 1 \text{ MHz}, V_{GS} = 0$		3260		pF
C_{oss}	Output capacitance			640		pF
C_{rss}	Reverse Transfer Capacitance			110		pF
Q_g	Total gate charge	$V_{DD} = 160V, I_D = 75A,$		84		nC
Q_{gs}	Gate-source charge	$V_{GS} = 10V$		18		nC
Q_{gd}	Gate-drain charge	(see Figure 16)		34		nC

C_{oss} := 640pF

Output capacitance of the MOSFET

Table 5. Dynamic

Symbol	Parameter	Test conditions	Min.	Typ.	Max.	Unit
$g_{fs}^{(1)}$	Forward transconductance	$V_{DS} = 15V, I_D = 37A$		40		S
C_{iss}	Input capacitance			3260		pF
C_{oss}	Output capacitance	$V_{DS} = 25V, f = 1 \text{ MHz}, V_{GS} = 0$		640		pF
C_{rss}	Reverse Transfer Capacitance			110		pF
Q_g	Total gate charge	$V_{DD} = 160V, I_D = 75A,$		84		nC
Q_{gs}	Gate-source charge	$V_{GS} = 10V$		18		nC
Q_{gd}	Gate-drain charge	(see Figure 16)		34		nC

Vdrive := 10V

Drive voltage applied to the MOSFET gate. This is the regulation of the small buck converter.

trise := 33ns

Rise time of the MOSFET

tfall := 29ns

Fall time of the MOSFET

Table 6. Switching times

Symbol	Parameter	Test conditions	Min.	Typ.	Max.	Unit
$t_{d(on)}$	Turn-on delay time	$V_{DD} = 100V, I_D = 37A$		53		ns
t_r	Rise time	$R_G = 4.7\Omega, V_{GS} = 10V,$		33		ns
$t_{d(off)}$	Turn-off delay time	$(see \text{ } Figure \text{ } 15)$		75		ns
t_f	Fall time			29		ns

Inductor Parameter

In selecting inductors, the RMS and peak current are useful parameters. Select and inductor that has higher RMS current rating than the computed RMS current above. The saturation current of the inductor must be higher than the peak or maximum current computed above.

RDC := 0.00286Ω

maximum DC resistance of the inductor

Part number ¹	Inductance ² ±10% (μH)		DCR ³ (mOhms) nom max		SRF typ ⁴ (MHz)	Isat (A) ⁵			Irms (A) ⁶	
	10%	20%	30%	20°C rise	40°C rise					
SER2915L-152KL	1.5	1.50	1.65	60	100	>100	>100	>100	20	30
SER2915H-222KL	2.2	1.86	2.05	40	100	>100	>100	>100	20	30
SER2915L-222KL	2.2	1.50	1.65	50	82.0	84.0	84.8	84.8	20	30
SER2918H-332KL	3.3	2.60	2.86	40	91.0	92.5	93.6	93.6	20	28
SER2915H-332KL	3.3	1.86	2.05	30	62.0	66.9	68.4	68.4	20	30
SER2915L-332KL	3.3	1.50	1.65	40	48.0	54.0	57.0	57.0	20	30
SER2918H-472KL	4.7	2.60	2.86	30	59.0	61.2	62.4	62.4	20	28
SER2915H-472KL	4.7	1.86	2.05	25	42.0	48.0	50.1	50.1	20	30
SER2915L-472KL	4.7	1.50	1.65	30	33.0	36.9	39.0	39.0	20	30
SER2918H-682KL	6.8	2.60	2.86	25	42.0	45.0	45.9	45.9	20	28
SER2915H-682KL	6.8	1.86	2.05	20	30.0	34.5	36.2	36.2	20	30
SER2915L-682KL	6.8	1.50	1.65	25	22.0	26.0	27.8	27.8	20	30
SER2918H-103KL	10	2.60	2.86	20	28.0	31.2	32.1	32.1	20	28
SER2915H-103KL	10	1.86	2.05	15	18.0	21.5	23.4	23.4	20	30
SER2915L-103KL	10	1.50	1.65	20	13.0	16.2	17.6	17.6	20	30
SER2918H-153KL	15	2.60	2.86	16	18.0	21.2	21.9	21.9	20	28
SER2915H-153KL	15	1.86	2.05	12	11.5	14.0	15.2	15.2	20	30
SER2915L-153KL	15	1.50	1.65	15	7.5	9.8	11.0	11.0	20	30
SER2918H-223KL	22	2.60	2.86	15	12.0	14.0	15.0	15.0	20	28
SER2915H-223KL	22	1.86	2.05	10	7.0	8.6	9.6	9.6	20	30
SER2915L-223KL	22	1.50	1.65	10	4.5	6.0	6.8	6.8	20	30
SER2918H-333KL	33	2.60	2.86	10	7.0	8.7	9.6	9.6	20	28
SER2915H-333KL	33	1.86	2.05	8	4.0	5.1	5.9	5.9	20	30
SER2915L-333KL	33	1.50	1.65	7	2.0	2.6	3.3	3.3	20	30

Output Capacitor Stress

In selecting output capacitors, the ripple current and voltage must be considered. The computed ripple current above is the total ripple current. That will be divided by the number of parallel output capacitors used.

Cout_parallel := 4

Iripple_capability := 1.6A

$$\text{Ioutcap_Vinmax_stress} := \frac{\frac{\text{Irip_outcap_Vinmax}}{\text{Cout_parallel}}}{\text{Iripple_capability}}$$

Ioutcap_Vinmax_stress = 92.214.%

$$\text{Ioutcap_Vinmin_stress} := \frac{\frac{\text{Irip_outcap_Vinmin}}{\text{Cout_parallel}}}{\text{Iripple_capability}}$$

Ioutcap_Vinmin_stress = 84.189.%

MOSFET Power Loss and Stress Calculation

Q1 MOSFET

Maximum Input Voltage

Q1_parallel := 2

$$\text{Idrain_Q1_Vinmax} := \frac{\text{I}_{\text{RMS_Q1_Vinmax}}}{\text{Q1_parallel}}$$

Idrain_Q1_Vinmax = 4.519 A

This is the number of MOSFETs used in the Q1 slot. If only one MOSFET is used, put here 1.

This is the computed drain current from above derivations. If you are going to use several MOSFETs in Q1 slot, divide this by the number of MOSFETs you use.

$$\text{Pconduction_Q1_Vinmax} := \text{Idrain_Q1_Vinmax}^2 \cdot \text{RDson} \cdot \text{RDson_norm}$$

Pconduction_Q1_Vinmax = 1.111 W

This is the individual conduction loss or the RDson loss of the MOSFETs in Q1 slot

$$Ploss_Qgtotal_Q1_Vinmax := \frac{1}{2} Qgtotal \cdot Vdrive \cdot Fsw$$

Ploss_Qgtotal_Q1_Vinmax = 0.059 W

This is the loss on individual MOSFETs on Q1 slot due to the total gate charge

$$Ploss_Coss_Q1_Vinmax := \frac{1}{2} \cdot Coss \cdot VQ1_Vinmax^2 \cdot Fsw$$

Ploss_Coss_Q1_Vinmax = 0.448 W

This is the individual loss on the MOSFETs in Q1 slot due to output capacitance

$$Ploss_trise_tfall_Q1_Vinmax := \frac{1}{2} \cdot (trise + tfall) \cdot Idrain_Q1_Vinmax \cdot Vdrive \cdot Fsw$$

Ploss_trise_tfall_Q1_Vinmax = 0.196 W

This is the individual loss on the MOSFETs in the Q1 slot due to the rise and fall time delays

$$\begin{aligned} Ploss_total_Q1_Vinmax := & Pconduction_Q1_Vinmax + Ploss_Qgtotal_Q1_Vinmax \\ & + Ploss_Coss_Q1_Vinmax + Ploss_trise_tfall_Q1_Vinmax \end{aligned}$$

Ploss_total_Q1_Vinmax = 1.814 W

This is the total power loss or power dissipation of each MOSFETs in the Q1 slot.

Minimum Input Voltage

$$Idrain_Q1_Vinmin := \frac{I_{RMS_Q1_Vinmin}}{Q1_parallel}$$

Idrain_Q1_Vinmin = 5.793 A

This is the computed drain current from above derivations. If you are going to use several MOSFETs in Q1 slot, divide this by the number of MOSFETs you use.

$$Pconduction_Q1_Vinmin := Idrain_Q1_Vinmin^2 \cdot RDson \cdot RDson_norm$$

Pconduction_Q1_Vinmin = 1.826 W

This is the individual conduction loss or the RDson loss of the MOSFETs in Q1 slot

$$Ploss_Qgtotal_Q1_Vinmin := \frac{1}{2} Qgtotal \cdot Vdrive \cdot Fsw$$

Ploss_Qgtotal_Q1_Vinmin = 0.059 W

This is the loss on individual MOSFETs on Q1 slot due to the total gate charge

$$P_{loss_Coss_Q1_Vinmin} := \frac{1}{2} \cdot C_{oss} \cdot V_{Q1_Vinmin}^2 \cdot F_{sw}$$

Ploss_Coss_Q1_Vinmin = 0.161 W

This is the individual loss on the MOSFETs in Q1 slot due to output capacitance

$$P_{loss_trise_tfall_Q1_Vinmin} := \frac{1}{2} \cdot (t_{rise} + t_{fall}) \cdot I_{drain_Q1_Vinmin} \cdot V_{drive} \cdot F_{sw}$$

Ploss_trise_tfall_Q1_Vinmin = 0.251 W

This is the individual loss on the MOSFETs in the Q1 slot due to the rise and fall time delays

$$\begin{aligned} P_{loss_total_Q1_Vinmin} := & P_{conduction_Q1_Vinmin} + P_{loss_Qgtotal_Q1_Vinmin} \dots \\ & + P_{loss_Coss_Q1_Vinmin} + P_{loss_trise_tfall_Q1_Vinmin} \end{aligned}$$

Ploss_total_Q1_Vinmin = 2.297 W

This is the total power loss or power dissipation of each MOSFETs in the Q1 slot.

Q2 MOSFET

Maximum Input Voltage

Q2_parallel := 3

$$I_{drain_Q2_Vinmax} := \frac{I_{RMS_Q2_Vinmax}}{Q2_parallel}$$

I_{drain}_Q2_Vinmax = 6.084 A

This is the number of MOSFETs used in the Q1 slot. If only one MOSFET is used, put here 1.

This is the computed drain current from above derivations. If you are going to use several MOSFETs in Q1 slot, divide this by the number of MOSFETs you use.

$$P_{conduction_Q2_Vinmax} := I_{drain_Q2_Vinmax}^2 \cdot R_{DSon} \cdot R_{DSon_norm}$$

Pconduction_Q2_Vinmax = 2.014 W

This is the individual conduction loss or the RDSon loss of the MOSFETs in Q1 slot

$$P_{loss_Qgtotal_Q2_Vinmax} := \frac{1}{2} Q_{gtotal} \cdot V_{drive} \cdot F_{sw}$$

Ploss_Qgtotal_Q2_Vinmax = 0.059 W

This is the loss on individual MOSFETs on Q1 slot due to the total gate charge

$$P_{loss_Coss_Q2_Vinmax} := \frac{1}{2} \cdot C_{oss} \cdot V_{Q2_Vinmax}^2 \cdot F_{sw}$$

Ploss_Coss_Q2_Vinmax = 0.448 W

This is the individual loss on the MOSFETs in Q1 slot due to output capacitance

$$P_{loss_trise_tfall_Q2_Vinmax} := \frac{1}{2} \cdot (t_{rise} + t_{fall}) \cdot I_{drain_Q2_Vinmax} \cdot V_{drive} \cdot F_{sw}$$

Ploss_trise_tfall_Q2_Vinmax = 0.264 W

This is the individual loss on the MOSFETs in the Q1 slot due to the rise and fall time delays

$$\begin{aligned} P_{loss_total_Q2_Vinmax} := & P_{conduction_Q2_Vinmax} + P_{loss_Qgtotal_Q2_Vinmax} \dots \\ & + P_{loss_Coss_Q2_Vinmax} + P_{loss_trise_tfall_Q2_Vinmax} \end{aligned}$$

Ploss_total_Q2_Vinmax = 2.784 W

This is the total power loss or power dissipation of each MOSFETs in the Q1 slot.

Minimum Input Voltage

$$I_{drain_Q2_Vinmin} := \frac{I_{RMS_Q2_Vinmin}}{Q2_parallel}$$

I_{drain_Q2_Vinmin} = 5.525 A

This is the computed drain current from above derivations. If you are going to use several MOSFETs in Q1 slot, divide this by the number of MOSFETs you use.

$$P_{conduction_Q2_Vinmin} := I_{drain_Q2_Vinmin}^2 \cdot RDSon \cdot RDSon_norm$$

Pconduction_Q2_Vinmin = 1.661 W

This is the individual conduction loss or the RDSon loss of the MOSFETs in Q1 slot

$$P_{loss_Qgtotal_Q2_Vinmin} := \frac{1}{2} Q_{gtotal} \cdot V_{drive} \cdot F_{sw}$$

Ploss_Qgtotal_Q2_Vinmin = 0.059 W

This is the loss on individual MOSFETs on Q1 slot due to the total gate charge

$$P_{loss_Coss_Q2_Vinmin} := \frac{1}{2} \cdot C_{oss} \cdot V_{Q2_Vinmin}^2 \cdot F_{sw}$$

Ploss_Coss_Q2_Vinmin = 0.161 W

This is the individual loss on the MOSFETs in Q1 slot due to output capacitance

$$P_{loss_trise_tfall_Q2_Vinmin} := \frac{1}{2} \cdot (t_{rise} + t_{fall}) \cdot I_{drain_Q2_Vinmin} \cdot V_{drive} \cdot F_{sw}$$

Ploss_trise_tfall_Q2_Vinmin = 0.24 W

This is the individual loss on the MOSFETs in the Q1 slot due to the rise and fall time delays

$$\begin{aligned} P_{loss_total_Q2_Vinmin} := & P_{conduction_Q2_Vinmin} + P_{loss_Qgtotal_Q2_Vinmin} \dots \\ & + P_{loss_Coss_Q2_Vinmin} + P_{loss_trise_tfall_Q2_Vinmin} \end{aligned}$$

Ploss_total_Q2_Vinmin = 2.121 W

This is the total power loss or power dissipation of each MOSFETs in the Q1 slot.

Heat Sink Sizing

Equation to Use

$$P_{diss} = \frac{T_{j_max} - T_{case_max}}{R_{thjc} + R_{thchs}}$$

Where ;

Pdiss is the computed power dissipation of the MOSFET

T_{j_max} is the maximum ambient temperature

T_{case_max} is the maximum case temperature setting

R_{thjc} is the thermal resistance from junction to case

R_{thchs} is the thermal resistance from case to heat sink

Solve for heat sink thermal resistance

$$P_{diss} = \frac{T_{j_max} - T_{case_max}}{R_{thjc} + R_{thchs}} \text{ solve } , R_{thchs} \rightarrow \frac{T_{j_max} - T_{case_max}}{P_{diss}} - R_{thjc}$$

T_{case_max} := 100Δ°C

This is a good case temperature regulation for the MOSFETs. Usually MOSFETs are operated with this case temp. Although some cases that MOSFETs are allowed to go to 120°C, but here let us consider 100°C only for enough margin.

$$R_{thjc} := 0.66 \frac{\Delta^\circ C}{W}$$

Thermal Resistance

	Parameter	Typ.	Max.	Units
R_{thjc}	Junction-to-Case	—	0.50	°C/W
R_{thcs}	Case-to-Sink, Flat, Greased Surface	0.24	—	
R_{thja}	Junction-to-Ambient	—	40	

$$R_{thchs_Q1_Vinmax} := -R_{thjc} - \frac{T_{case_max} - 175 \cdot \Delta^\circ C}{P_{loss_total_Q1_Vinmax}}$$

$$R_{thchs_Q1_Vinmax} = 40.685 \frac{1}{W} \cdot \Delta^\circ C$$

This should be the maximum thermal resistance of the heat sink for each MOSFET on Q1 slot when maximum input voltage is used

$$R_{thchs_Q1_Vinmin} := -R_{thjc} - \frac{T_{case_max} - 175 \cdot \Delta^\circ C}{P_{loss_total_Q1_Vinmin}}$$

$$R_{thchs_Q1_Vinmin} = 31.986 \frac{1}{W} \cdot \Delta^\circ C$$

This should be the maximum thermal resistance of the heat sink for each MOSFET on Q1 slot when minimum input voltage is used

$$R_{thchs_Q2_Vinmax} := -R_{thjc} - \frac{T_{case_max} - 175 \cdot \Delta^\circ C}{P_{loss_total_Q2_Vinmax}}$$

$$R_{thchs_Q2_Vinmax} = 26.275 \frac{1}{W} \cdot \Delta^\circ C$$

This should be the maximum thermal resistance of the heat sink for each MOSFET on Q2 slot when maximum input voltage is used

$$R_{thchs_Q2_Vinmin} := -R_{thjc} - \frac{T_{case_max} - 175 \cdot \Delta^\circ C}{P_{loss_total_Q2_Vinmin}}$$

$$R_{thchs_Q2_Vinmin} = 34.705 \frac{1}{W} \cdot \Delta^\circ C$$

This should be the maximum thermal resistance of the heat sink for each MOSFET on Q2 slot when minimum input voltage is used

The thermal resistance of the heat sink needed for maximum input voltage and minimum input voltage cannot co-exist. So, need to consider the smallest value. The heat sink to use must have a thermal resistance less than the computed smallest thermal resistance between Vinmax and Vinmin.

The computed minimum thermal resistance is 40.7'C/W. For more margin, we can use a heat sink with thermal resistance below 26 'C/W.

$$R_{thchs} := 8 \frac{\Delta^{\circ}\text{C}}{\text{W}}$$

This is the target maximum thermal resistance of the heat sink. The lower is the better.

Note: A heat sink with smaller thermal resistance has a larger surface area.

MOSFET Power Capability

In this analysis, the MOSFETs are mounted on a PCB without using a heat sink. There is a form of heat sink but only limited by the PCB trace/pads. To minimize the thermal resistance from junction to ambient, the pad area must be large enough. This analysis is more applicable to SMD MOSFETs.

$$T_{j_max} := 150\Delta^{\circ}\text{C}$$

This is the maximum junction temperature the MOSFET can operate

$$P_{capability_MOSFET} := \frac{T_{j_max} - T_{case_max}}{R_{thjc} + R_{thchs}}$$

$$P_{capability_MOSFET} = 5.774 \text{ W}$$

This is the maximum power capability of the selected MOSFET given the above parameters

$$P_{stress_Q1_Vinmax} := \frac{P_{loss_total_Q1_Vinmax}}{P_{capability_MOSFET}}$$

$$P_{stress_Q1_Vinmax} = 31.418\%$$

This is the power stress of each of the MOSFETs in Q1 slot at maximum input voltage

$$P_{stress_Q1_Vinmin} := \frac{P_{loss_total_Q1_Vinmin}}{P_{capability_MOSFET}}$$

$$P_{stress_Q1_Vinmin} = 39.791\%$$

This is the power stress of each of the MOSFETs in Q1 slot at minimum input voltage

$$P_{stress_Q2_Vinmax} := \frac{P_{loss_total_Q2_Vinmax}}{P_{capability_MOSFET}}$$

Pstress_Q2_Vinmax = 48.227-%

This is the power stress of each of the MOSFETs in Q2 slot at maximum input voltage

$$P_{stress_Q2_Vinmin} := \frac{P_{loss_total_Q2_Vinmin}}{P_{capability_MOSFET}}$$

Pstress_Q2_Vinmin = 36.732-%

This is the power stress of each of the MOSFETs in Q2 slot at minimum input voltage

Inductor Power Loss

Inductor power loss is composed of DC and AC components. DC loss is due to the DC resistance while AC loss is due to the core losses (hysteresis and eddy current loss). In most cases, the DC and AC losses are almost in the same magnitude for switching frequency of 100 kHz to 200kHz so whatever the computed DC loss is can be multiplied by two to get the total loss. A margin is can be added as well.

$$P_{loss_L1_Vinmax} := I_{RMS_L1_Vinmax}^2 \cdot R_{DC}$$

Ploss_L1_Vinmax = 1.186 W

$$P_{loss_L1_Vinmin} := I_{RMS_L1_Vinmin}^2 \cdot R_{DC}$$

Ploss_L1_Vinmin = 1.17 W

Total Inductor Loss

$$P_{loss_L1_Vinmax_total} := 3 \cdot P_{loss_L1_Vinmax}$$

Ploss_L1_Vinmax_total = 3.559 W

In this analysis, the switching frequency is set to 650kHz. It is expected that the AC loss is high, so it is approximated as twice the DC loss.

$$P_{loss_L1_Vinmin_total} := 3 \cdot P_{loss_L1_Vinmin}$$

Ploss_L1_Vinmin_total = 3.509 W

Efficiency Computations

$$\text{Efficiency} = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{out} + P_{loss}} = \frac{P_{in} - P_{loss}}{P_{in}}$$

Below equation is to be used in the computations of efficiency because the input power is the one being regulated.

$$\text{Efficiency} = \frac{P_{in} - P_{loss}}{P_{in}}$$

$$\begin{aligned} P_{loss_total_Vinmax} := & Q1_{parallel} \cdot P_{loss_total_Q1_Vinmax} + Q2_{parallel} \cdot P_{loss_total_Q2_Vinmax} \dots \\ & + P_{loss_L1_Vinmax_total} \end{aligned}$$

$$P_{loss_total_Vinmax} = 15.541 \text{ W}$$

$$\begin{aligned} P_{loss_total_Vinmin} := & Q1_{parallel} \cdot P_{loss_total_Q1_Vinmin} + Q2_{parallel} \cdot P_{loss_total_Q2_Vinmin} \dots \\ & + P_{loss_L1_Vinmin_total} \end{aligned}$$

$$P_{loss_total_Vinmin} = 14.467 \text{ W}$$

$$\text{Efficiency_Vinmax} := \frac{P_{in} - P_{loss_total_Vinmax}}{P_{in}}$$

$$\text{Efficiency_Vinmax} = 96.115\%$$

This is the efficiency of the power section at max Vin

$$\text{Efficiency_Vinmin} := \frac{P_{in} - P_{loss_total_Vinmin}}{P_{in}}$$

$$\text{Efficiency_Vinmin} = 96.383\%$$


This is the efficiency of the power section at min Vin


Dead Time Calculation

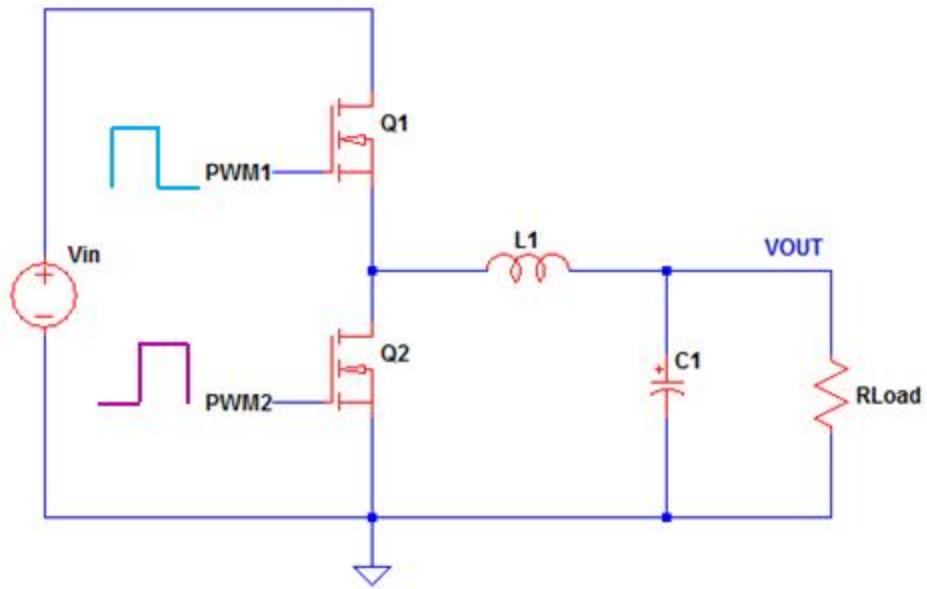Q2 Should turn ON only after Q1 is fully turned OFF. The same scenario, Q1 should turn ON only after Q2 is fully turn OFF.

The total turn OFF delay of Q1 will be the sum of controller execution delay (from code to pin realization), driver propagation delay and Ciss discharge plus others as specified in the datasheet.

The total delay to turn OFF Q2 is the same with Q1 considering the same MOSFET to use.



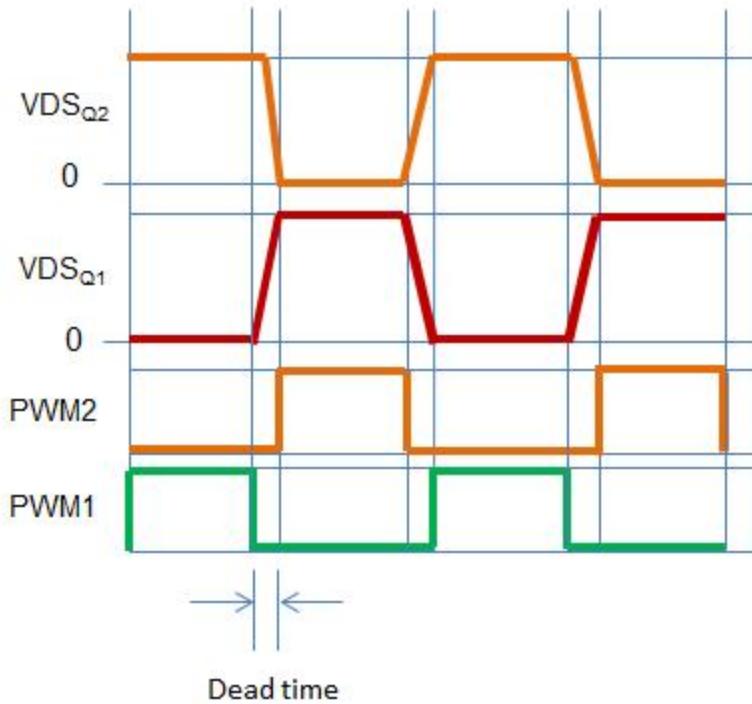

CISS Discharge

$$V_{GS_Q1} = V_{GS_Q1_initial} \cdot e^{\frac{-t_{decay_Q1gate}}{(RgQ1 + RgDriver) \cdot CISS_Q1}}$$

$$t_{decay_Q1gate} = -CISS_Q1 \cdot \ln\left(\frac{V_{GS_Q1}}{V_{GS_Q1_initial}}\right) \cdot (RgQ1 + RgDriver)$$

Where;

$V_{GS_Q1_initial}$ - is the applied VGS when Q1 is running ON

t_{decay_Q1gate} - is the time delay when the charge voltage in the CISS is below the minimum VGS threshold of Q1

$RgQ1$ - is the gate resistance of Q1. This is the sum of the external gate resistance and the internal resistance on the IC

$RgDriver$ - gate pull down resistance of the driver

$CISS_Q1$ - input capacitance of Q1

VGS_Q1_initial := Vdrive

CISS_Q1 := 3260pF

Cstray := 10nF

Estimated stray capacitance

VGSThreshold_min := 2V

VGS_Q1 := VGSThreshold_min

RgQ1 := 5Ω

RgDriver := 2.5Ω

$$t_{decay_Q1gate} := -(CISS_Q1 + Cstray) \cdot \ln\left(\frac{VGS_Q1}{VGS_Q1_initial}\right) \cdot (RgQ1 + RgDriver)$$

$$t_{decay_Q1gate} = 160.059 \cdot ns$$

The MOSFET datasheet specifies a turn off delay. There is no information if this is already covering the CISS discharge, so we just add this to the computed value above.

Total Turn OFF Delay of Q1

MCUdelay := 100ns

MCU delay from code to pin realization

driver_delay := 45ns

Driver propagation delay

toffQ1 := 75ns

Specified turn off delay of Q1 in the datasheet

$$toff_delay_Q1_total := MCUdelay + driver_delay + t_{decay_Q1gate} + toffQ1$$

$$toff_delay_Q1_total = 380.059 \cdot ns$$

This is the computed dead time with estimated stray capacitance

Dead Time

margin := 30%

deadtime := (1 + margin)toff_delay_Q1_total

deadtime = 494.076·ns

Starting dead time. For verification in actual unit since the stray capacitances are difficult to estimate.